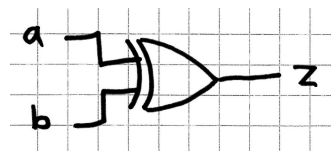

Digital Systems: Problem sheet 5


Mike Spivey, Hilary Term, 2019

- 1 An XOR gate $z = a \oplus b$ has the following truth table:

a	b	z
0	0	0
0	1	1
1	0	1
1	1	0



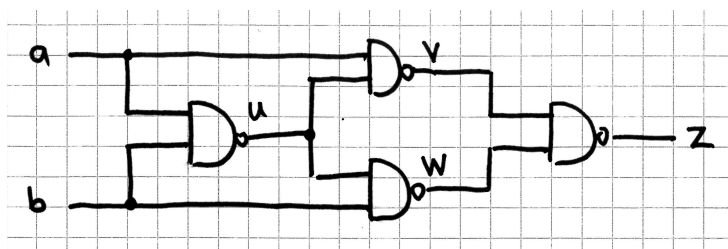- (a) Show that \oplus is associative and commutative. Does it have an identity element?
- (b) Show how to build an XOR gate from a 2-input OR gate, two 2-input AND gates and two inverters.
- (c) Can you still build an XOR gate if one of the two AND gates is replaced by an OR gate?
- (d) Show that the following circuit of four NAND gates also computes $z = a \oplus b$.



- 2 (a) Design a CMOS implementation of a NOR gate, with the following truth table.

a	b	z
0	0	1
0	1	0
1	0	0
1	1	0

2 Digital Systems: Problem sheet 5

- (b) In the lecture, we designed a CMOS gate that computed the function

$$z = \neg((a \wedge b) \vee c).$$

Design a gate that computes

$$w = \neg((a \vee b) \wedge c)$$

instead.


- (c) What general principle underlies relates parts (a) and (b) of this question with the CMOS NAND and AND-OR-NOT gates designed in the lectures?

- 3 (a) Design a *clocked set/reset latch* with the following behaviour. There are two inputs a and b ; if $a = 1$ at a clock edge, then the output z goes from 0 to 1. The output then remains at 1 until $b = 1$ at a clock edge, and then returns to 0. The behaviour if $a = b = 1$ at any clock edge can be whatever is easiest to implement.

- (b) Enhance your design to produce an additional output w that receives a pulse for exactly one clock cycle whenever the circuit is triggered by an event with $a = 1$, but does not receive another pulse until the circuit has been reset by setting $b = 1$ at a clock edge.

- 4 A T-type flip-flop has a control input t , in addition to an edge-triggered clock input. If $t = 1$ at a clock edge, then the flip-flop changes state; otherwise it remains in the same state.

q_t	t	q_{t+1}
0	0	0
0	1	1
1	0	1
1	1	0

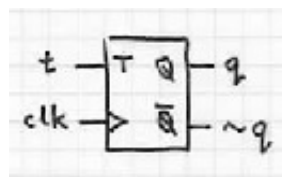

- (a) Show how to construct a T-type flip-flop from a D-type flip-flop and an XOR gate.
- (b) Show how to construct a synchronous binary counter from a row of T-type flip-flops and a row of AND gates.
- (c) Show how to construct a synchronous binary counter from a row of D-type flip-flops and a row of half-adders.
- (d) Use your answer to part (a) to explain the connection between the circuit in parts (b) and (c).

- 5 Tests with an actual pull-cord light switch installed at the lecturer's home reveal that the light does not go on until the cord is released, but goes off as soon as it is pulled a second time. Modify the bathroom light-switch circuit to reproduce this behaviour.

- 6 In the lecture, it was shown that the set of connectives $\{\wedge, \vee, \neg\}$ is adequate to express any Boolean function, as is the singleton set $\{\text{NAND}\}$.

- (a) Show that the singleton $\{\text{NOR}\}$ is also adequate.
- (b) Show that the set $\{\text{XOR}, \neg\}$ is *not* adequate. *Hint: find a proper subset of the set of all Boolean functions of two variables x and y that contains x , y and the two Boolean constants and is closed under XOR and \neg .*